

## Assignment 8 - Building a Controller

50 Points Possible

11/4/2024

Attempt 1



10/31/2024

NEXT UP: Review Feedback

Attempt 1 Score:

N/A



Add Comment

Unlimited Attempts Allowed

▼ Details

## 8 Building a Controller

In this assignment, we will finish our implementation of a fully-functioning (albeit limited) CPU by adding a Controller component.



## Objectives

1. Understand the various control signals throughout the architecture
2. Combine previous skills in combinatorial logic to create the controller

## Resources

[Assignment8.circ](https://usu.instructure.com/courses/759913/files/92989942?wrap=1) (<https://usu.instructure.com/courses/759913/files/92989942?wrap=1>)

([https://usu.instructure.com/courses/759913/files/92989942/download?download\\_frd=1](https://usu.instructure.com/courses/759913/files/92989942/download?download_frd=1))

[ControlSimple.txt](https://usu.instructure.com/courses/759913/files/92989945?wrap=1) (<https://usu.instructure.com/courses/759913/files/92989945?wrap=1>)

([https://usu.instructure.com/courses/759913/files/92989945/download?download\\_frd=1](https://usu.instructure.com/courses/759913/files/92989945/download?download_frd=1))

[ControlAdvanced.txt](https://usu.instructure.com/courses/759913/files/92989947?wrap=1) (<https://usu.instructure.com/courses/759913/files/92989947?wrap=1>)

([https://usu.instructure.com/courses/759913/files/92989947/download?download\\_frd=1](https://usu.instructure.com/courses/759913/files/92989947/download?download_frd=1))

## Task 1 - Create the Controller

**Overview:** In this task you will be using combinatorial logic to create a controller component. Use the following resources to help complete this controller. You should implement it as a subcircuit named Controller.

**Instruction Formats:**

Name	Bit Fields					Notes (16 bits total)
	bits 15-12	bits 11-9	bits 8-6	bits 5-3	bits 2-0	
R-Format	op	rs	rt	rd	funct	Arithmetic, logic
I-Format	op	rs	rt	address/ immediate (6 bits)		Load/store, branch, immediate
J-Format	op	target address (12 bits)				Jump




**Opcodes:**

Core Instruction Set	Syntax	Format	Op	funct
<b>add</b>	add	R	0000	010
<b>subtract</b>	sub	R	0000	110
<b>and</b>	and	R	0000	000
<b>or</b>	or	R	0000	001
<b>set less than</b>	slt	R	0000	111
<b>load word</b>	lw	I	0001	xxx
<b>store word</b>	sw	I	0010	xxx
<b>branch on equal</b>	beq	I	0011	xxx
<b>add immediate</b>	addi	I	0101	xxx

## Control Signals:

Signal Name	Effect when deasserted (0)	Effect when asserted(1)
<b>RegWrite</b>	Register does not change	Register is written with data from <b>Write Data</b>
<b>ALUSrc</b>	Operand 2 comes from Register File	Operand 2 comes from immediate
<b>ALU Operation</b>	What operation the ALU performs	
<b>MemWrite</b>	We do not write to data memory	We do write to data memory
<b>MemtoReg</b>	ALU Result flows back to register file	Memory value flows back to register file
<b>Branch</b>	0 indicates we do not have a beq instruction	1 indicates we do have a beq instruction
<b>RegDst</b>	Write Register comes from the <b>rt</b> field	Write Register comes from the <b>rd</b> field

## CPU Diagram (for 32-bit MIPS):

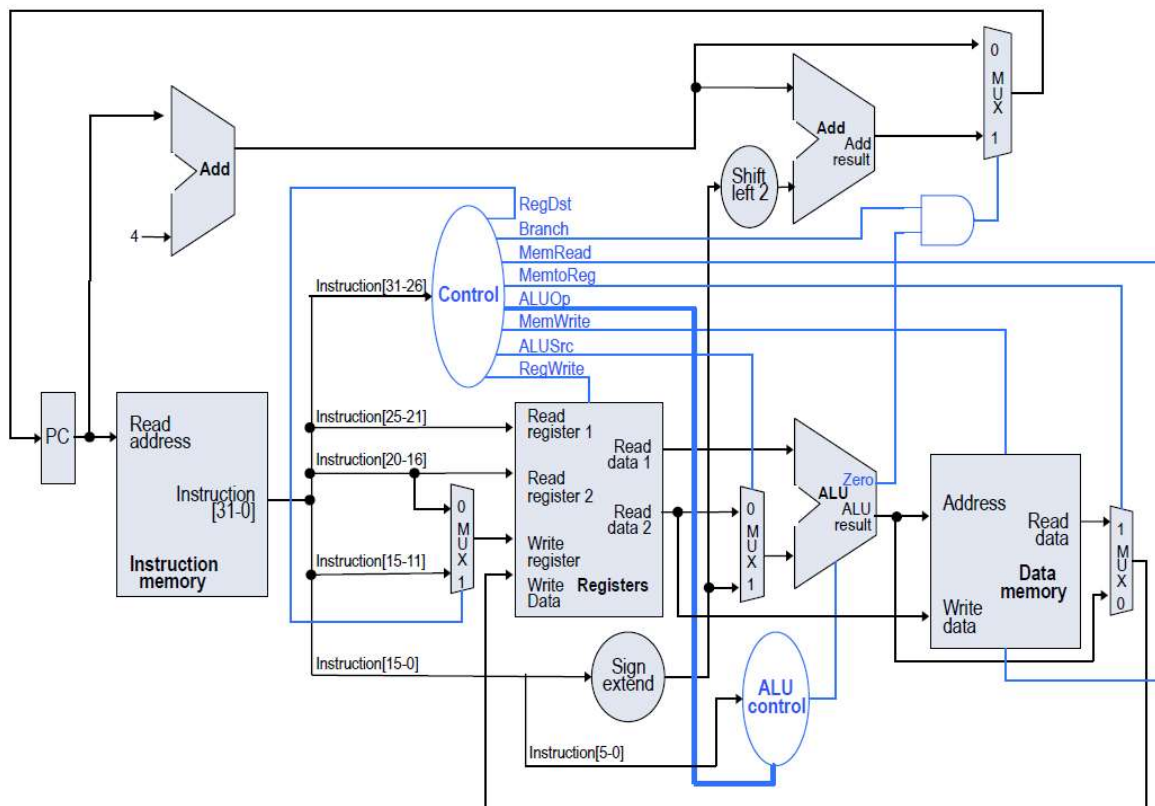

### Inputs:

- 4-bit Opcode (this should come from the instruction)
- 3-bit function code (this should come from the funct field of the instruction)

### Outputs:

- 1-bit RegDst
- 1-bit Branch
- 1-bit MemRead
- 1-bit MemtoReg
- 3-bit ALUOp
- 1-bit MemWrite
- 1-bit ALUSrc
- 1-bit RegWrite

### Tips:

- Start by creating 4-way AND gates that match the Opcode for each instruction
  - These AND gates should output 1 if the Opcode matches the one for each instruction
  - For example, you should have an **AND** gate labeled "lw", that only activates if the Opcode is 0001
  - Really helps to use the **Negate Input** attribute of the AND gates for this
- Once you have each of these gates setup, you can begin connecting their output to the output pins
- For example, **MemWrite** should be 1 if you are writing to memory, i.e. a **sw** instruction. Note that some outputs (**RegWrite** for example), is activated by several instructions. You will need to use an additional gate in this case.
- You can handle all of the outputs except for **ALUOp** by using the above process.
- For **ALUOp**, it should follow the following process:
  - If the instruction is an **R-type** instruction, **ALUOp** should just be whatever **funct** is

- Otherwise, there are two other options for the **ALUOp**
  - The opcode for **add**: 010
  - The opcode for **sub**: 110
  - You will need to figure out which instructions send the code for add vs. subtract to **ALUOp**
- Use multiplexers to enable all of the above behavior
- Take this task one control signal at a time
  - For each control signal, ask yourself the following:
    - What does it mean when the control signal is 1?
    - Which instructions set the control signal to 1?
    - What opcodes do these control signals have?
    - How can I match those opcodes with combinational logic (AND gates and OR gates)?
- You will only use the **funct** field when determining the 3-bit **ALUOp** output.

### Testing

The following test vector files can be used to test your implementation of the Controller component

**ControlSimple.txt**: This file will test all of the outputs **except** for **ALUOp**.

**ControlAdvanced.txt**: This file will test all of the outputs.




### Submission

Submit a file named **Assignment8.circ** containing your Controller implementation.

#### ✓ View Rubric

#### Assignment 10

Criteria	Ratings		Pts
Task 1 - Controller <a href="#">view longer description</a>	50 pts Full Marks	0 pts No Marks	/ 50 pts
			Total Points: 0

 

Preview Unavailable

Assignment8.circ



 [Download](#)

([https://usu.instructure.com/files/93047155/download?download\\_frd=1&verifier=5IS0KmeHZZcgN4bfvDxISJkzb6Rg99CN6v5iCuHy](https://usu.instructure.com/files/93047155/download?download_frd=1&verifier=5IS0KmeHZZcgN4bfvDxISJkzb6Rg99CN6v5iCuHy))

<

(<https://usu.instructure.com/courses/759913/modules/items/6509937>)

>

Attempt

(<https://usu.instructure.com/courses/759913/modules/items/6509937>)

